
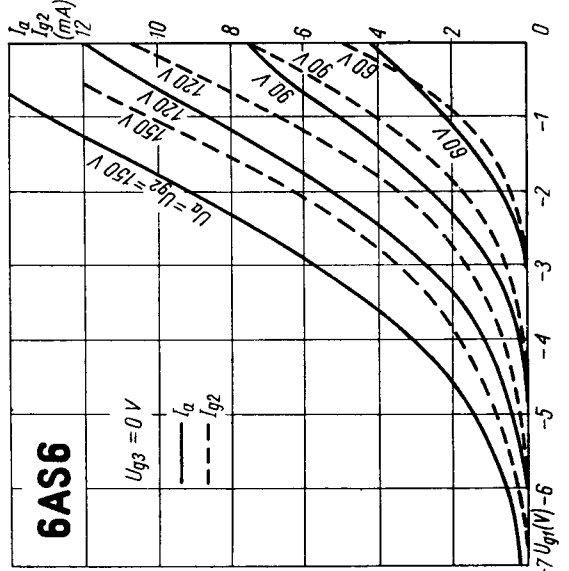
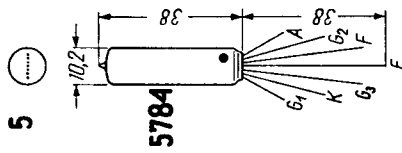
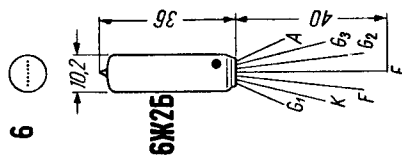
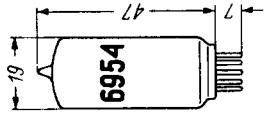
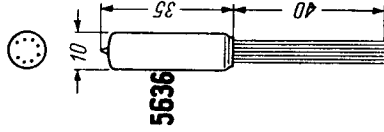


T.	Image	Image	U _f	I _f	U _o	U _{g2}	U _{g3}	U _{g1}	I _o	I _{g2}	S _(g1/o)		S _(g3/a)	R _i	R _k	U _{flk}	I _k	P _a	P _{g2}		
											mA/V	mA/V								MΩ	Ω
6 AS 6 5725 ¹⁾ 5784 6486	int	1	6,3	0,175	120	120	0	- 2	5,2	3,5	3,2	0,47	0,15								
	int	2	6,3	0,175	120	120	- 3	- 2	3,6	4,8	1,85	0,8									
	amer	5	6,3	0,2	120	120	0	- 10	0,1												
	amer	3	6,3	0,2	120	120	- 15		0,02												
6 Ж 2 Б	CCCP	6	6,3	0,2	120	120	0	- 2	5,5	2,5	3,2	0,8	0,8		200						
					120	120	- 3		0,02												
					120	120	- 15														
					125	125															
6 Ж 2 II	CCCP	2	6,3	0,175	120	120	0	- 2,3	4	1,5	3,7	0,5	0,075	200							
					120	120	- 3														
					120	120	- 15														
					150	150															
6 Ж 10 Б	CCCP	6	6,3	0,25	120	120	0	- 1,5	12	8	4,5		0,35								
					120	120	- 3														
					120	120	- 15														
					150	150															
5636 ²⁾	int	4	6,3	0,15	100	100	0	- 1,5	5,6	4	3,2	0,5	0,11	150							
					100	100	- 1		4	5,8	1,95	0,95									
					100	100	0	- 7,5	0,01												
					100	100	- 8		0,01												
6954	int	2	6,3	0,3	100	100	15		3,5	5,7	1,28	0,32	0,32	(Mixer, f _{max} = 400 MHz)							
					100	100	- 8														
					155	155															
					165	165															
					150	150	3	- 1	5,8	6,6	2,05	1	0,05								
					150	150	- 9,5		0,1												
					150	150		- 6,5	0,01												
					300	300															


¹⁾ vide * 4, a, b, c, f, g (U_f = 6,3 V ± 10%)
²⁾ vide * 4, a, b, c, d, e, f, g (U_f = 6,3 V ± 5%)
³⁾ vide * 4, a, b, g (U_f = 6,3 V ± 10%)

Equivalents

CK 624 AX	Ray = 5784	GL-5725 ¹⁾	GE = 5725	6 AS 6W ³⁾	amer = 6 AS 6	5784 WA ²⁾	int = 5784
CK 5725 ¹⁾	Ray = 5725	M 8196 ³⁾	Mul = 6 AS 6	6 F 33	Tes = 6 AS 6	6150	amer = 5784
CK 5784	Ray = 5784	R 271	SFR = 5784	624 AX	Ray = 5784	6187	amer = 5725
CK 5784 WA ²⁾	Ray = 5784	WL-6954	Wst = 6954	409 A	WE = 6 AS 6	6486-A	amer = 6486
EF 730	Mul = 5636	6 AS 6 S ¹⁾	eur = 6 AS 6	5636-A ³⁾	RCA = 5636	7752	amer = 6 AS 6

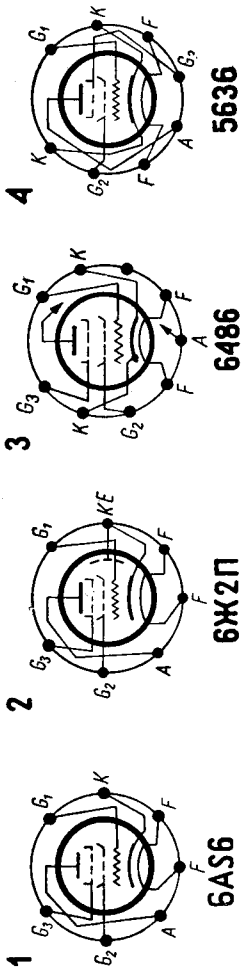


6AS6

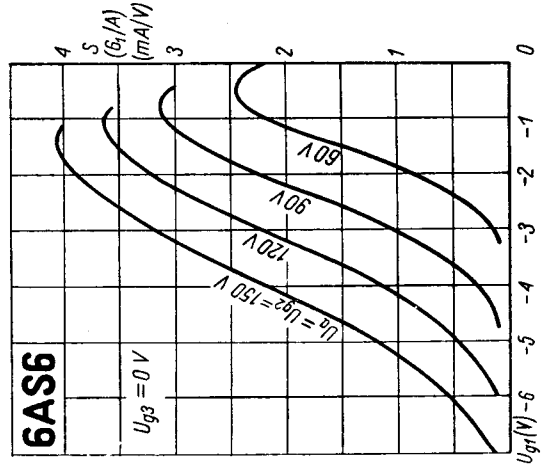

6AS6

T.	$C_{g1/k}$	$C_{a/k}$	$C_{g1/a}$	$C_{g3/a}$	$C_{g3/g1}$	$C_{g3/a+g_2+g_3+k}$	vide
	pF	pF	pF	pF	pF	pF	
6 AS 6	{ 3,9 4	2,2 3	0,025 0,02	0,7 0,7	0,15 0,15	3,3 3,4	*5 *6
6Ж2Б	4,9	4,1	0,03				*6
6 Ж2П	4,5	2,5	0,02				*5
5636	{ 4 4	1,9 3,4	0,034 0,02	1,1 1,1	0,17 0,15	3,8 4	*5 *6
5725	3,9	3	0,02		0,15		*6
5784	4,5	3,6	0,03				*6
6150	4,5	3,6	0,03				*6
6954	6	5	0,0035	1,5	0,09	3	*5

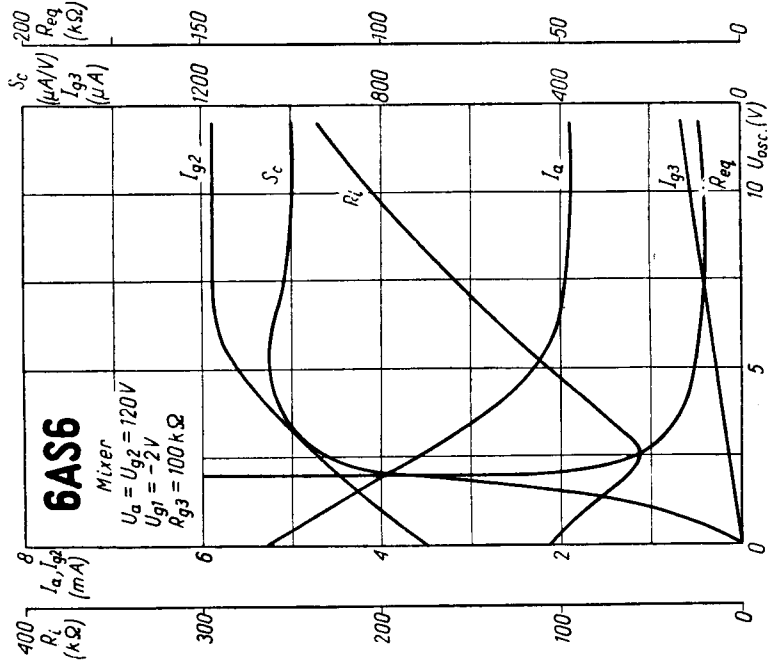

6AS6 Mixer

$U_a = U_{g2} = 120V$
 $U_{g1} = -2V$
 $R_{g3} = 100 k\Omega$

